

DIGITAL QUESTIONS

OCT-17-2001

ASIC WORLD
Directory

Digital

Tutorial

Questions

Tools

Books


Links

Home


Disclaimer

Sample Digital Questions Asked in Interviews

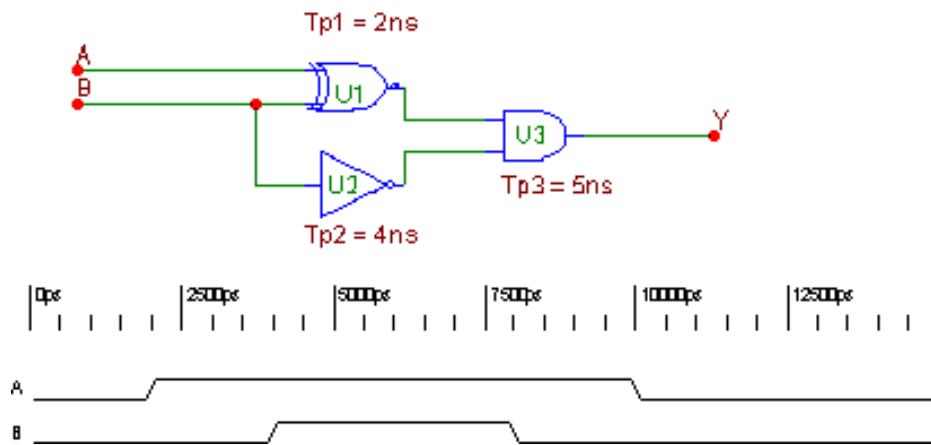
- What is the output of AND gate in the circuit below, when A and B are as in waveform? Where, T_p is gate delay of respective gate.



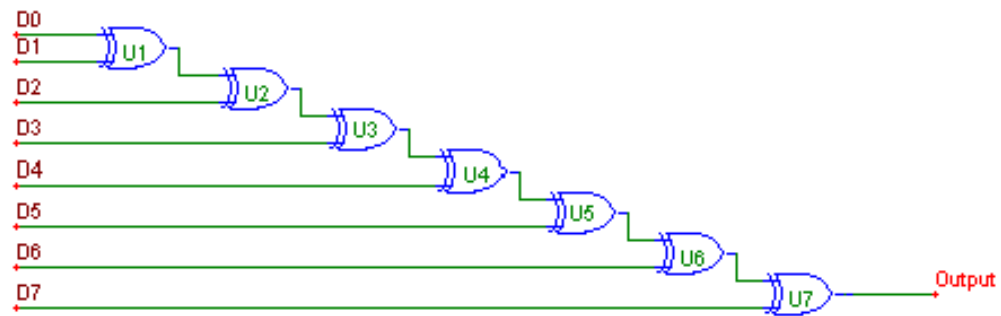
- Identify the below circuit, and its limitation ?



 - What is the current through the resistor R1 (I_c) ?




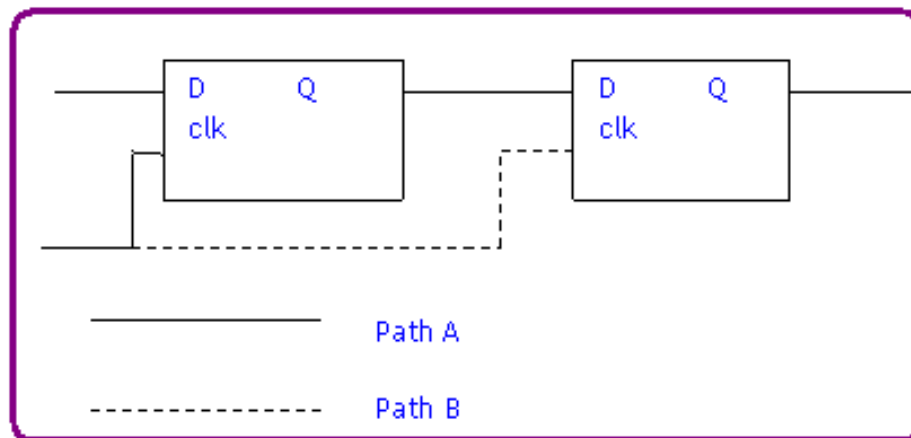- ❖ Referring to the diagram below, briefly explain what will happen if the propagation delay of the clock signal in path B is much too high compare to path A. How do we solve this problem if the propagation delay of path B can not be reduced ?




- ❖ What is the function of a D flip-flop, whose inverted output is connected to its input ?
- ❖ Design a circuit to divide input frequency by 2 ?
- ❖ Design a divide-by-3 sequential circuit with 50% duty cycle.?
- ❖ What are the different types of adder implementation ?
- ❖ Draw a Transmission Gate-based D-Latch ?
- ❖ Give the truth table for a Half Adder. Give a gate level implementation of the same.

 
- ❖ What is the purpose of the buffer in below circuit, is it necessary/redundant to have buffer ?



 
- ❖ What is output of the below circuit, assuming that value of 'X' is not known ?



 - ❖ Consider a circular disk as shown in figure below with two sensors mounted X, Y and blue shade painted on the disk for a angle of 45 degree. Design a circuit with minimum number of gates to detect the direction of rotation.




- ❖ Design a OR gate from 2:1 MUX.


 


What is the difference between a LATCH and a FLIP-FLOP ?

 - Latch is a level sensitive device and flip-flop is edge sensitive device
- Latch is sensitive to glitches on enable pin, where as flip-flop is immune to glitches.
- Latches take less gates (also less power) to implement then flip-flops
- Latches are faster then flip-flops



Design a D Flip-Flop from two latches.

  


- ◆ Design a 2 bit counter using D Flip-Flop.

Transition Table ➡ Next State Transition Table ➡ K-map ➡ circuit


- ◆ What are the two types of delays in any digital system ?

Wire Delay and Gate Delay

 - ◆ Design a Transparent Latch using a 2:1 Mux.



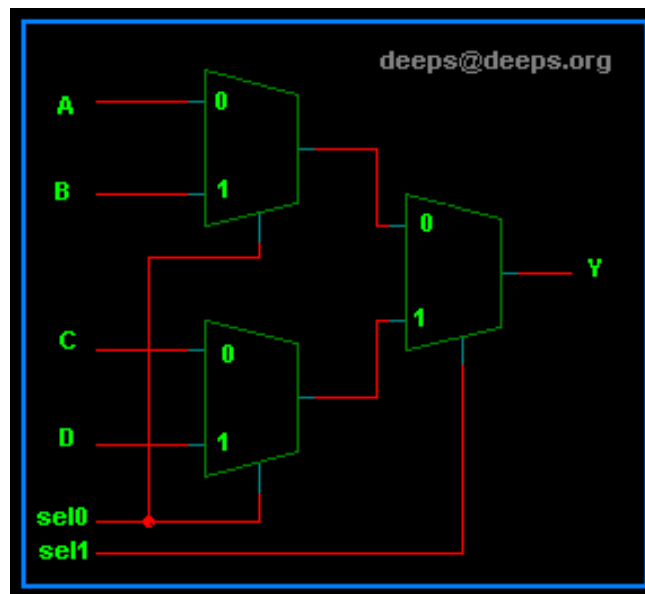- ◆ Design a 4:1 Mux using 2:1 Mux's and some combo logic.



- ◆ What is metastable state ? How does it occur ?

[Refer Tidbits section](#)

- ◆ What is metastability ?

[Refer Tidbits section](#)

- ◆ Design a 3:8 decoder
- ◆ Design a FSM to detect sequence "101" in input sequence.
- ◆ Convert NAND gate into Inverter, in two different ways.
- ◆ Design a D and T flip flop using 2:1 mux, use of other components not allowed, just the mux.
- ◆ Design a divide by two counter using D-Latch.
- ◆ Design D Latch from SR flip-flop.
- ◆ Define Clock Skew , Negative Clock Skew, Positive Clock Skew ?
- ◆ What is Race Condition ?
- ◆ Design a 4 bit Gray Counter ?
- ◆ Design 4-bit Synchronous counter, Asynchronous counter ?
- ◆ Design a 16 byte Asynchronous FIFO?
- ◆ What is the difference between a EEPROM and FLASH ?
- ◆ What is the difference between a NAND-based Flash and NOR-based Flash ?
- ◆ You are given a 100 MHz clock , Design a 33.3 MHz clock with and without 50 % duty cycle?
- ◆ Design a Read on Reset System ?
- ◆ Which one is superior Asynchronous Reset or Synchronous Reset, Explain ?
- ◆ Design a State machine for Traffic Control at a Four point Junction ?



Copyright © 1998-2004
Deepak Kumar Tala - All rights reserved
Do you have any Comments? mail me at: deepak@asic-world.com