

# **UnnaTI Analog Program Reference Material**

# UnnaTI Analog Program


## Syllabus for screening:

- ☐ KCL & KVL
- ☐ Thevenin & Norton theorems
- ☐ Superposition concepts
- ☐ R-C circuits time constant/ waveform
- ☐ Final conditions for R-C circuits
- ☐ Charge conservation in a capacitor
- ☐ Inductance concepts
- ☐ Controlled sources
- ☐ Periodic waveforms
- ☐ Laplace domain
- ☐ Differential equations
- ☐ Probability
- ☐ Permutation & Combination
- ☐ Data analysis and interpretation
- ☐ Digital gates - Boolean algebra


## Points to note:

- ☐ Use the provided notes to get a feel for what the screening test will be like
- ☐ If you spot any errors in the notes, please bring it to the notice of [saivarun@ti.com](mailto:saivarun@ti.com)
- ☐ Actually screening will be multiple choice format
- ☐ You will be tested on the understanding of basic concepts

# KCL, KVL

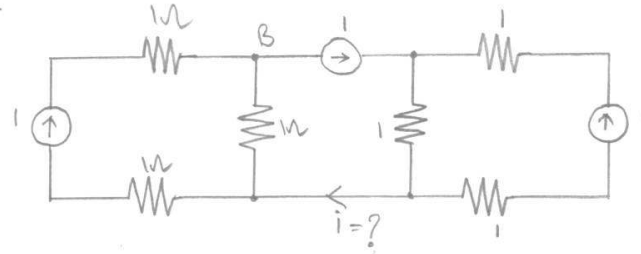① KCL

Solution

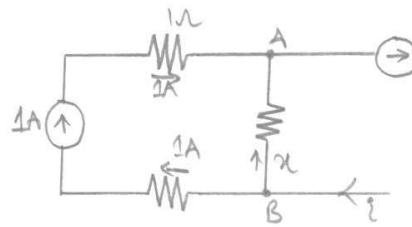

Applying KCL at node B

$$i - 1 - x = 0$$

$$x = i - 1 \quad \text{--- ①}$$

Applying KCL at node A

$$1 + x - 1 = 0$$

$$x = 0 \quad \text{--- ②}$$


Equating ① and ②

$$i - 1 = 0$$


$$\Rightarrow i = 1$$

Simple solution :

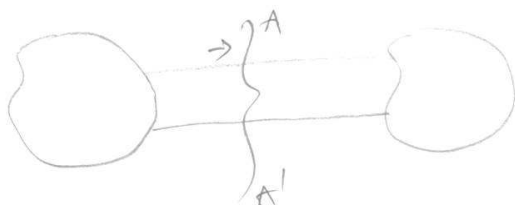KCL states at any node that sum of total incoming current is equal to sum of total outgoing current. Applying the same law across any plane: AA'




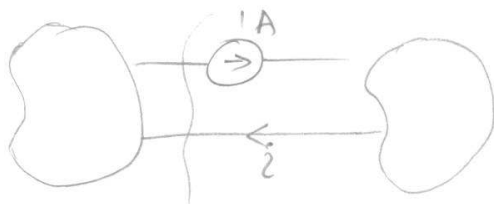total current coming in  $AA' =$  total current going out  $AA'$



from this principle  $i = 1$

Other example

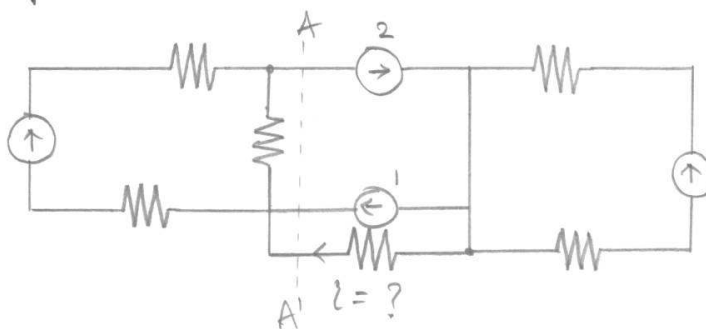


Across  $AA'$

$$2 - 1 - i = 0$$


$$i = 1$$

2. find  $V_x$  in the following circuit

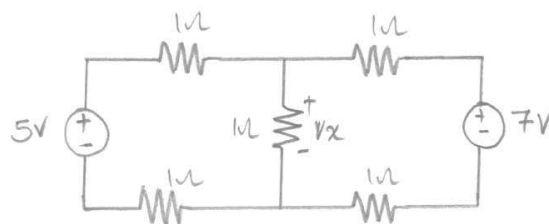

Solution :

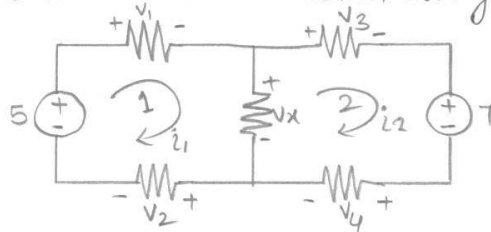Above circuit can be solved using loop analysis (KVL)



Applying KVL in loop 1:

$$V_1 + V_x + V_2 - 5 = 0 \quad \text{--- (1)}$$

(Observe that sign is used according to + or - appearing first on an element while traversing the loop)

Similarly for loop 2

$$V_3 + 7 + V_4 - V_x = 0 \quad \text{--- (2)}$$

Applying ohm's law:

$$V_1 = i_1 * 1, V_2 = i_1 * 1, V_3 = i_2 * 1, V_4 = i_2 * 1$$

Where as the current through the resistor across

which voltage drop is  $V_x = (i_1 - i_2) * 1$

$$V_x = (i_1 - i_2) * 1$$

Replacing  $V_1$  to  $V_o$  &  $V_x$  in ① & ②

$$i_1 + i_1 + (i_1 - i_2) - 5 = 0 \quad \text{--- ①A}$$

$$i_2 + 7 + i_2 - (i_1 - i_2) = 0 \quad \text{--- ②A}$$

Simplifying ①A & ②A

$$3i_1 - i_2 = 5 \quad \text{--- ①B}$$

$$-i_1 - 3i_2 = -7 \quad \text{--- ②B}$$

Solving ①B & ②B


$$i_2 = -2A, i_1 = 1A$$

Negative Sign for  $i_2$  means actual direction of current in loop2 is opposite to what is assumed

$$V_x = (i_1 - i_2) * 1 = [1 - (-2)] * 1 = 3V$$


KCL + KVL

3)

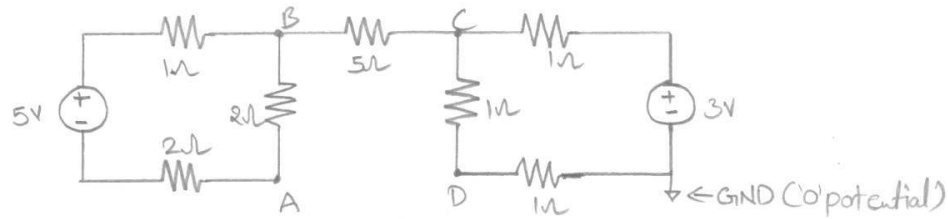

Find  $V_A$  (potential at node A) in the above circuit (with respect to ground)

Solution:

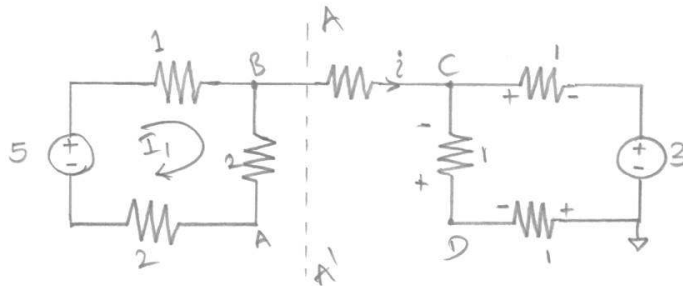

According to KCL, Current through  $5\Omega$  resistor (BC)  $i$  will be ZERO, as there is no path between AD for current to return

So,  $I_1$  loop 1 and loop 2 can be solved independently

Only purpose of  $5\Omega$  resistor is that  $V_B = V_C$

$$\text{Because } V_B - V_C = 5 \times i = 5 \times 0 = 0 \\ \Rightarrow V_B = V_C$$

In loop 2


$$i_2 \times 1 + 3 + i_2 \times 1 + i_2 \times 1 = 0$$

$$i_2 = \frac{-3}{3} = -1$$

$$V_C = 0 + 3 + i_2 \times 1$$

$$= 3 + (-1) \times 1 = 2$$

$$V_B = V_C = 2V$$

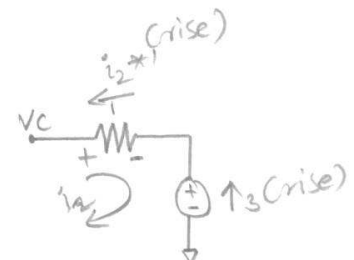




⑥

For loop ①, applying KVL

$$i_1 \times 1 + i_1 \times 2 + i_1 \times 2 - 5 = 0$$

$$5 i_1 = 5$$

$$i_1 = 1A$$

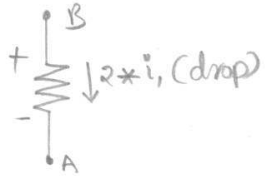

$$V_A = V_B - 2i_1$$


$$V_A = 2 - 2 \times 1$$

$$= 0V$$

# **Thevenin, Norton & Superposition Theorems**

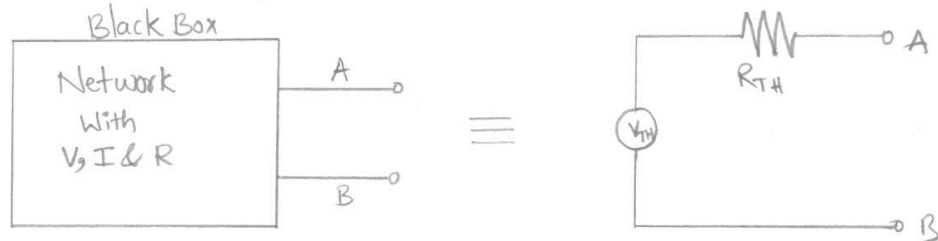
## Thevenin's theorem:

Any linear electrical network with any combination of voltage sources, current sources and resistances can be replaced at terminals A-B by an equivalent voltage source  $V_{TH}$  in series connection with equivalent resistance  $R_{TH}$ .



The theorem allows us to replace large network partially or completely with equivalent voltage source & series resistance to simplify the analysis


### Example:

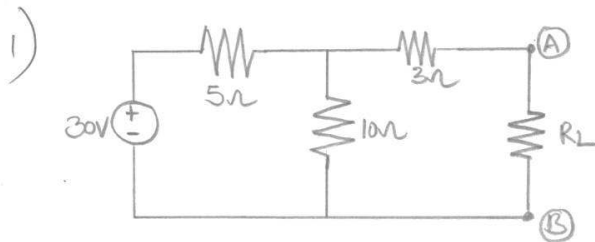

find  $V_{TH}$  &  $R_{TH}$  for above circuit

Step 1: Find  $V_{TH}$

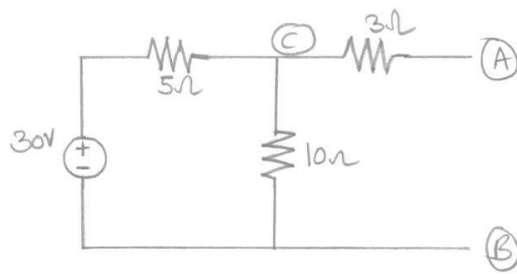To find  $V_{TH}$  open  $R_L$  terminals A & B have infinite resistance across them which means no current flows through them (A & B)



Note that no current flows through  $3\Omega$  resistor. Hence, nodes

Ⓐ & Ⓒ have same potential

By voltage division,


$$V_C = V_A = \frac{10}{15} \cdot 30 = 20V$$

$$\therefore V_{TH} = 20V$$

Step 2: Find  $R_{TH}$

To find  $R_{TH}$ , each independent source should be replaced with its internal resistance

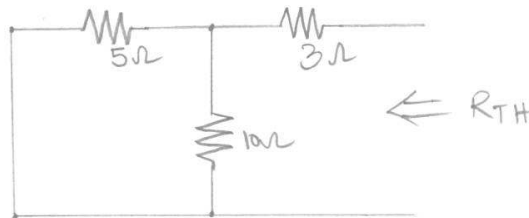
For ideal voltage source internal resistance is zero, while for ideal current source internal resistance is infinite. Hence, V source is replaced with short while current source with open circuit




$$R_{TH} = 3 + \left( \frac{5 \times 10}{5 + 10} \right) = 3 + 3.33$$

$$R_{TH} = 6.33\Omega$$

Equivalent Circuit  $\rightarrow$

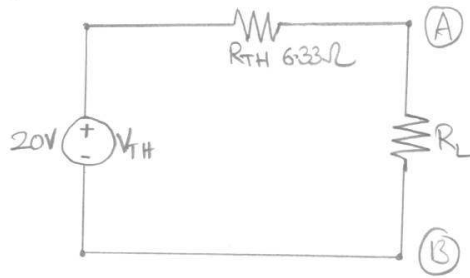

2) Find  $I_0$

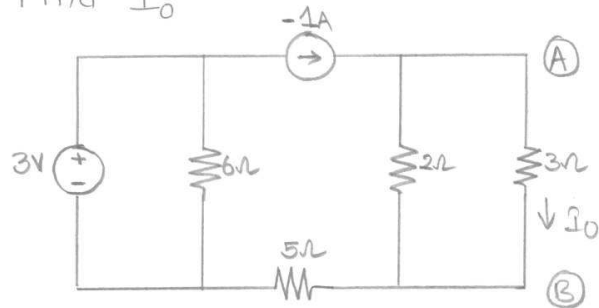

Step 1: Find  $V_{oc} = V_{AB}$


$V_{oc} \rightarrow$  open circuit voltage

Open  $3\Omega$  resistance

It is clear that  $-1A$  current flows via  $2\Omega$ . Hence  $V_{oc} = -2V$

(Note that -ve sign indicates potential at B is greater than A)

Step 2: Find  $R_{TH}$

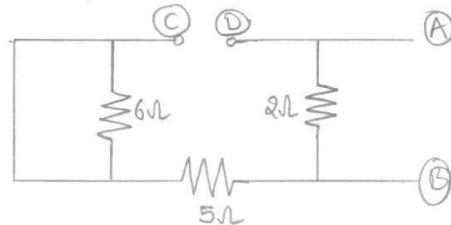

Note that circuit is open between C and D hence  $R_{TH} = 2\Omega$




Equivalent circuit

$$\text{Hence, } I_0 = \frac{-2}{5} = \underline{\underline{-0.4A}}$$


# Norton's Theorem

1)

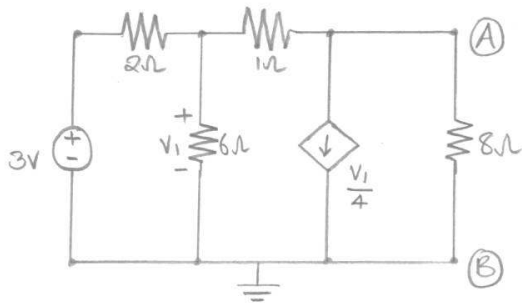

Find voltage across  $8\Omega$  resistor by Norton's theorem

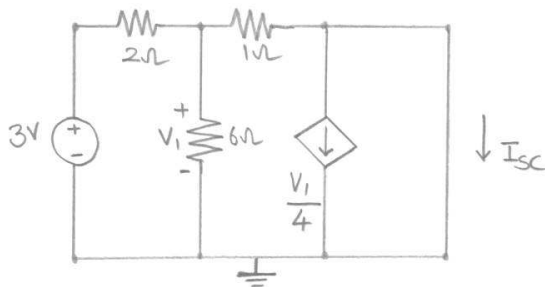Step 1: Short  $8\Omega$  resistor and find  $I_{sc}$




By KCL,  $\frac{3 - V_1}{2} = \frac{V_1}{1} + \frac{V_1}{6}$

$$\therefore \frac{3}{2} = \frac{10}{6} V_1 \Rightarrow V_1 = \frac{9}{10} \text{ V}$$

$$\therefore I_{sc} = \frac{V_1}{1} - \frac{V_1}{4} = \frac{3}{4} * \frac{9}{10} = \frac{27}{40}$$

$$= 0.675 \text{ A}$$

Step 2: find  $R_0$

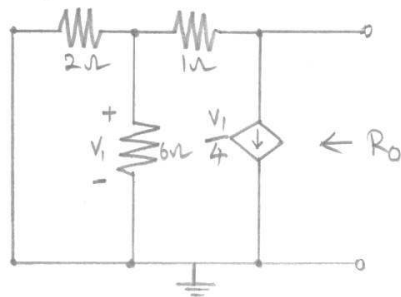


Note that only independent Sources are replacementd with their internal resistance

②

To find  $R_0$  we will add test source  $V_T$  at output & measure  $i_T$  Then

$$R_0 = \frac{V_T}{i_T}$$

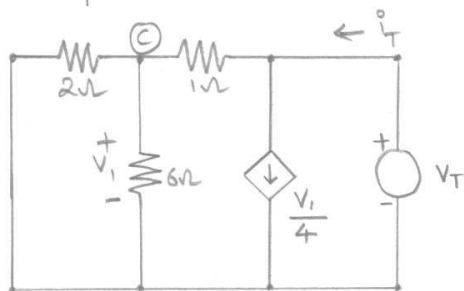

$$i_T = \frac{V_1}{4} + \frac{V_T - V_1}{1} \quad \text{--- (1)}$$


At node (C)  $\frac{V_T - V_1}{1} = \frac{V_1}{6} + \frac{V_1}{2}$

$$\therefore V_T = \frac{10}{6} V_1 \quad \therefore V_1 = \frac{6}{10} V_T$$

$$\therefore i_T = V_T - \frac{3}{4} V_1 = V_T - \frac{9}{20} V_T$$

$$\therefore R_0 = \frac{V_T}{i_T} = \frac{20}{11} \Omega = 1.82 \Omega$$

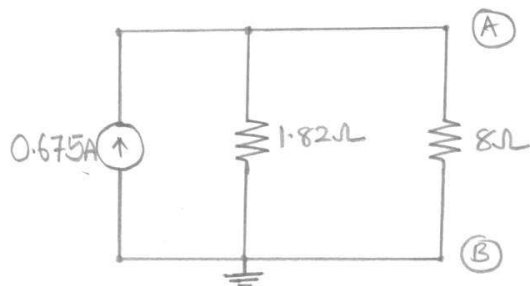$\therefore$  Norton's equivalent ckt is -




Hence, voltage across  $8\Omega$  resistor is -


$$V_{AB} = 0.675 (1.82 || 8) \\ \hat{=} 1V$$

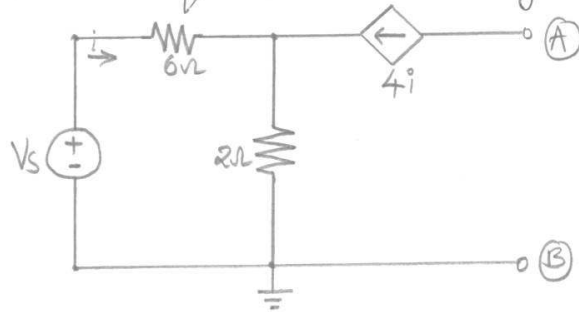(3)

Q) Find Norton's equivalent of following network. Comment on result



Step 1: Find  $I_{sc}$

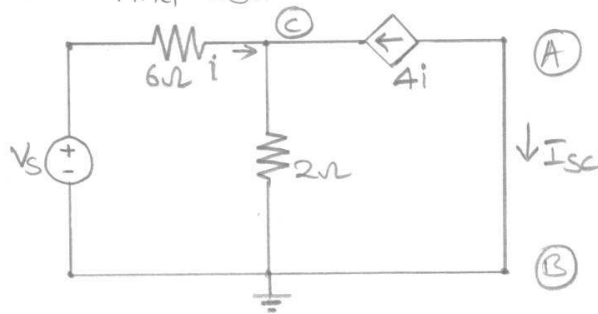

At node C,

$$V_C = 2(5i) = 10i$$


But,

$$i = \frac{V_S - V_C}{6}$$

$$\therefore i = \frac{V_S - 10i}{6}$$

$$\therefore I_{sc} = +i = \frac{V_S}{16}$$

Step 2: Find  $R_0$

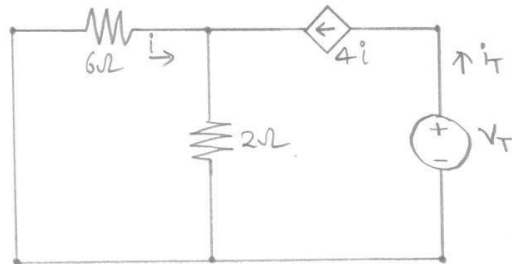

$V_T$  is test voltage source.


Note that current  $i_T = 4i$   
Hence  $i_T$  is independent of  $V_T$

$$\therefore R_0 = \frac{\Delta V_T}{\Delta i_T} = \infty \text{ (infinite)}$$



Hence, Norton's equivalent is

4

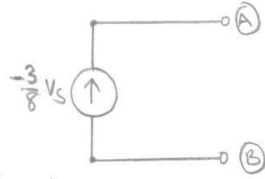


Clearly above circuit represents ideal Current Source


moreover, can you observe topological similarity with equivalent circuit of Common base amplifier

## Superposition Theorem:

i) Find 'v' using Superposition theorem:

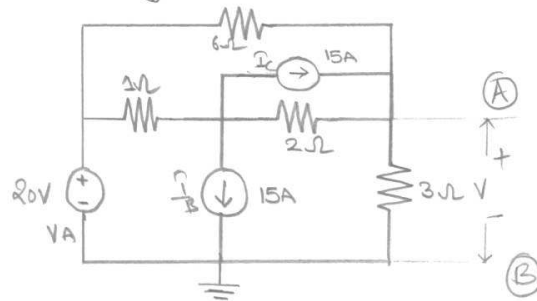

Step 1: Consider effect of only  $V_A$

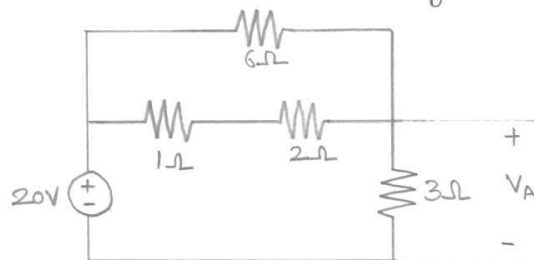


$$6 \parallel 3\Omega = 2\Omega$$

$$V_A = \frac{3}{2+3} \times 20$$

$$V_A = 12V$$

Step 2: Effect of  $I_B$  only

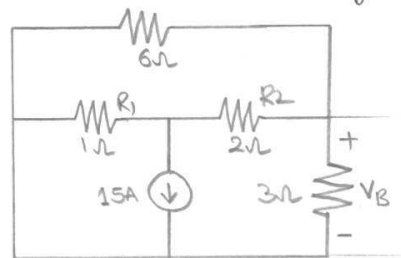

Note that  $3\Omega$  and  $6\Omega$  are in

Parallel

$$\therefore R_{\text{eff}}(\text{parallel } R) = 2\Omega$$

By current distribution current through  $R_2$

$$I_{R_2} = \frac{1}{1+4} \cdot (-15)$$

$$= -3A$$


This current flows through  $R_{\text{eff}}$  creating voltage drop  $V_B$

$$\therefore V_B = (-3A)(2\Omega) = -6V$$

Negative sign indicates polarity of  $V_B$  is opposite of Assumed Value.

(2)


Step 3: Effect of  $I_c$  Only

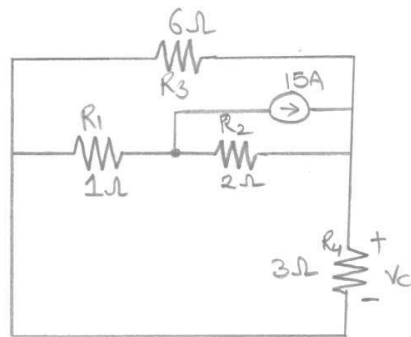

Note that  $R_3$  and  $R_4$  are in parallel

$$R_{eff} = R_3 \parallel R_4 = 2\Omega$$

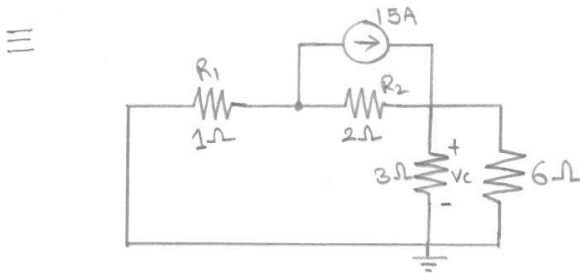Also, this  $R_{eff}$  is in series with  $R_1$  and  $(R_1 + R_{eff})$  is parallel to  $R_2$



By current division, Current through  $R_2$  is

$$\begin{aligned} I_{R_1} &= \frac{R_{eff} + R_1}{R_{eff} + R_1 + R_2} \cdot I_c \\ &= \frac{3}{5} \cdot 15 = 9A \end{aligned}$$


$$\therefore \text{Voltage } V_c = (15 - 9) \cdot 2 = 12V$$

Step 4: find voltage  $V_{AB}$  by addition of all components


$$\therefore V = V_A + V_B + V_c = 18V$$

(3)

2) Find  $i$  in following circuit:

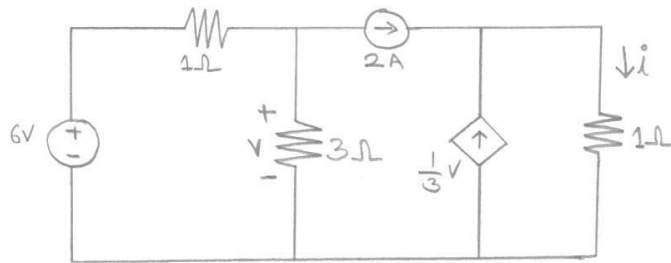


Step 1: Effect of 6V Source

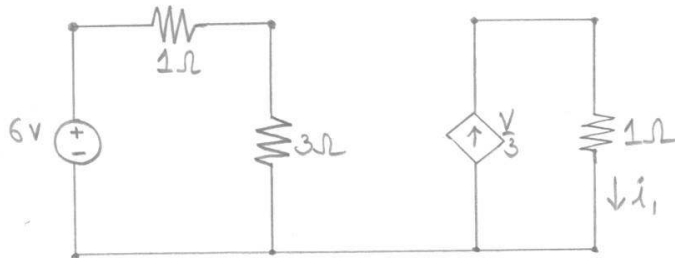

$$V = \frac{3}{1+3} \cdot 6 = 4.5 \text{ V}$$

$$\therefore i_1 = \frac{4.5}{3} = 1.5 \text{ A} \quad \text{--- (1)}$$

Step 2: Effect of 2A Source

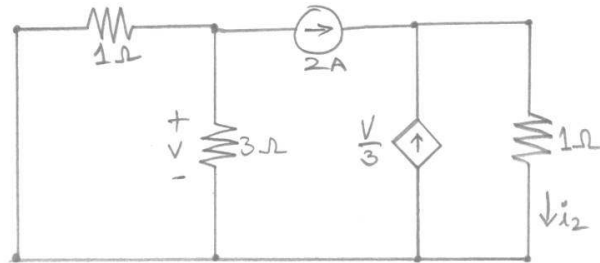

$$\text{Current through } 3\Omega \text{ resistor} = \frac{1}{1+3}(-2) = -0.5 \text{ A}$$

$$\therefore V = (-0.5)(3) = -1.5 \text{ V}$$

$$\therefore i_2 = 2 + \frac{-1.5}{3} = 1.5 \text{ A}$$

Step 3:

$$\text{Total Current by Superposition theorem} = i_1 + i_2 = 3 \text{ A}$$

# **Charge conservation in a capacitor**


①

## → Charge Conservation in a Capacitor

According to charge Conservation theory:

$$\boxed{\text{Initial charge} = \text{final charge}}$$

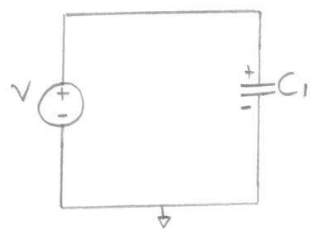
Consider a capacitor that is Connected to a voltage Source ( $V$ ) as shown below



In a steady state charge stored in capacitor is given by

$$\boxed{Q_1 = C_1 V}$$

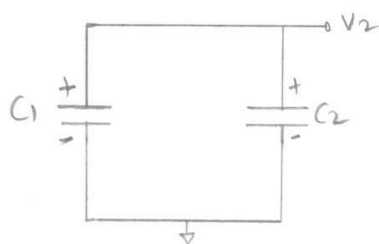Now Suppose this charged capacitor is disconnected from voltage source and connected back in parallel to another capacitor  $C_2$ ,



Charge stored in new configuration is →

$$Q_F = C_1 V_2 + C_2 V_2$$

By charge Conservation theory →

$$Q_I = Q_F$$



$$C_1 V = C_1 V_2 + C_2 V_2$$

Therefore  $V_2$  is given by →

$$\boxed{V_2 = \left( \frac{C_1}{C_1 + C_2} \right) \cdot V}$$

(2)

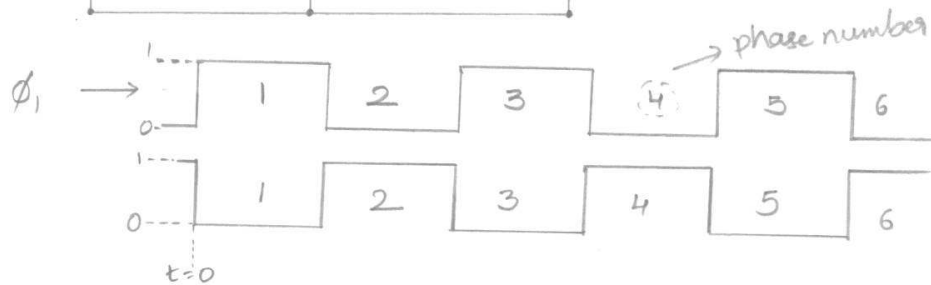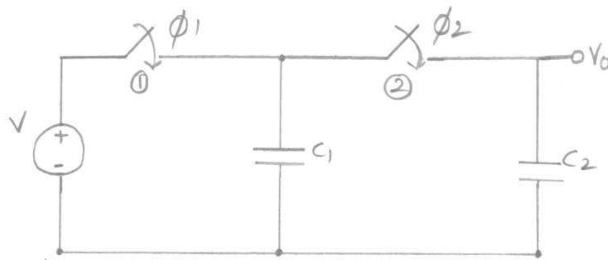
Q1. For below circuit calculate o/p voltage  $V_o \rightarrow$  with time



- Assume both the capacitors are charged to 0V at  $t=0$
- When  $\phi_1 = 1$ , Switch 1 will be ON  
 $\phi_1 = 0$ , Switch 1 will be OFF  
 Same is true for Switch 2

Sol)  $\rightarrow$  At phase 1  $\rightarrow$

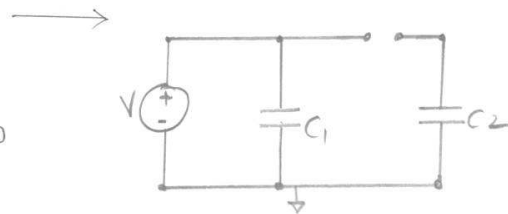
$$\begin{aligned} \text{Charge in } C_1 &\rightarrow C_1 \cdot V \\ C_2 &\rightarrow C_2 \times 0 = 0 \\ V_{o1} &\rightarrow 0 \end{aligned}$$



$\rightarrow$  At phase 2  $\rightarrow$

$$\text{Total charge} \rightarrow (C_1 + C_2) V_{o2}$$

By Charge Conservation theory

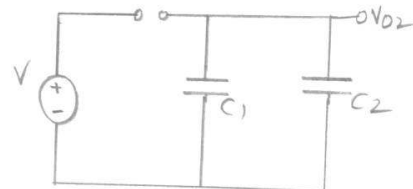

Charge in phase 1 = Charge in phase 2

$$C_1 V + 0 = (C_1 + C_2) V_{o2}$$

$$V_{o2} = \left( \frac{C_1}{C_1 + C_2} \right) V$$

(3)

At phase ③ →

$$\begin{aligned} \text{Charge in } C_1 &\rightarrow C_1 V \\ C_2 &\rightarrow C_2 V_{02} \end{aligned}$$

In this phase o/p voltage  $V_0$  will remain same as that of Phase 2, as there is no discharge path

$$V_{03} = \left( \frac{C_1}{C_1 + C_2} \right) V = V_{02}$$

$$\text{Total charge} = C_1 V + C_2 V_{02}$$

→ At phase ④ →

$$\text{Total charge} = (C_1 + C_2) V_{04}$$

$$\text{Charge in phase 3} = \text{charge in phase 4}$$

$$C_1 V + C_2 V_{02} = (C_1 + C_2) V_{04}$$

$$\therefore V_{04} = \frac{C_1}{C_1 + C_2} \cdot V + \frac{C_2}{C_1 + C_2} \cdot \left( \frac{C_1}{C_1 + C_2} \right) V$$

$$V_{04} = \frac{C_1}{C_1 + C_2} \left( 1 + \frac{C_2}{C_1 + C_2} \right) V$$

→ At phase ⑤ →

$$\begin{aligned} \text{Charge in } C_1 &= C_1 V \\ C_2 &= C_2 V_{04} \end{aligned}$$

$$\text{Total charge} = C_1 V + C_2 V_{04}$$

O/p voltage

$$\boxed{V_{05} = V_{04}}$$



(4)

→ At phase ⑥ →

$$\text{Total charge} = (C_1 + C_2) V_{06}$$

$$\text{Charge in phase 5} = \text{charge in phase 6}$$

$$C_1 V + C_2 V_{04} = (C_1 + C_2) V_{06}$$

$$\therefore V_{06} = \frac{V C_1}{C_1 + C_2} \left( 1 + \frac{C_2}{C_1} \cdot V_{04} \right)$$

$$V_{06} = \frac{V C_1}{C_1 + C_2} \left( 1 + \frac{C_2}{C_1 + C_2} + \left( \frac{C_2}{C_1 + C_2} \right)^2 \right)$$


→ At infinite phase →



$$V_{0,\infty} = \frac{V C_1}{C_1 + C_2} \left( 1 + \frac{C_2}{C_1 + C_2} + \left( \frac{C_2}{C_1 + C_2} \right)^2 + \left( \frac{C_2}{C_1 + C_2} \right)^3 + \dots \infty \right)$$

$$= V \cdot \frac{C_1}{C_1 + C_2} \cdot \frac{1}{1 - \frac{C_2}{C_1 + C_2}} = V$$

$$\therefore \boxed{V_{0,\infty} = V}$$

→ Below plot shows  $V_0$  V/s phase →

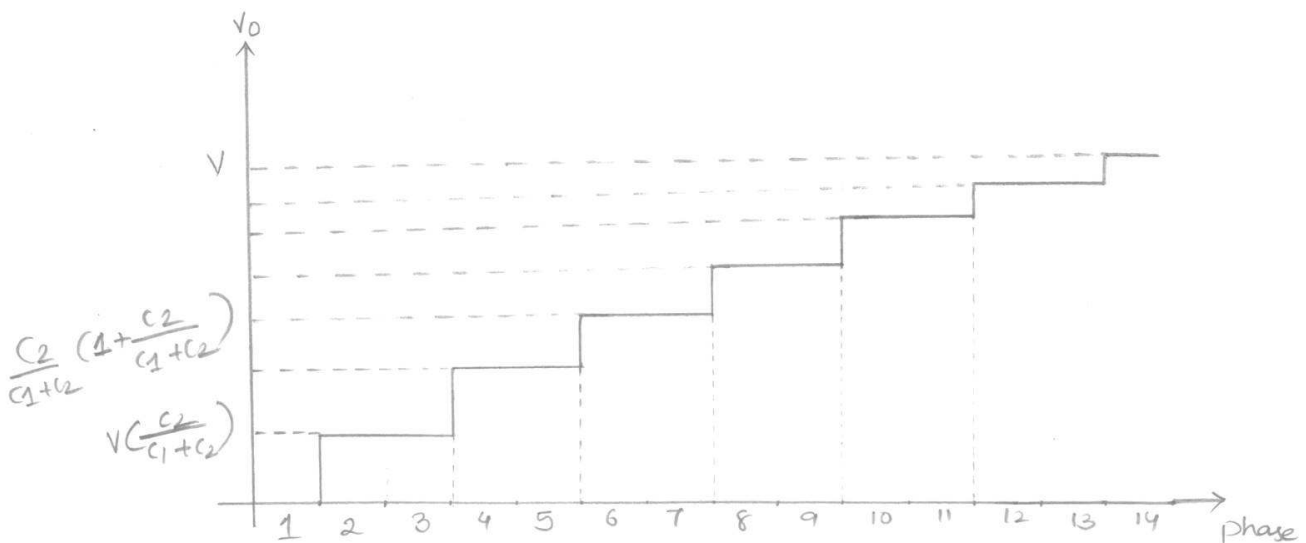

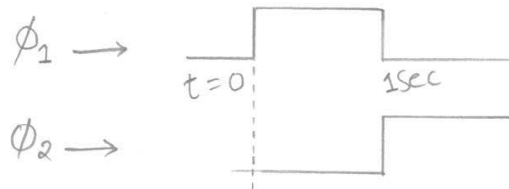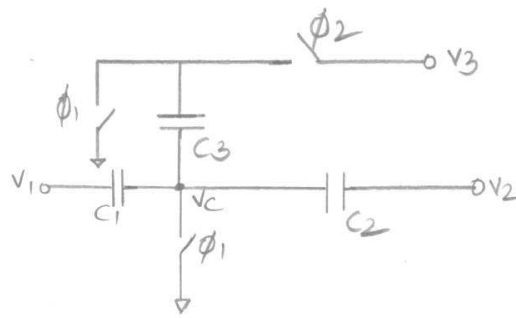Q<sub>2</sub>.

For the above circuit calculate voltage  $V_c$  at  $t = 1\text{sec}$

Sol<sup>n</sup>,

When  $\phi_1$  is high  $\rightarrow$

$$\begin{aligned}\text{Total charge} &= C_1(V_1 - 0) + C_2(V_2 - 0) + C_3(0 - 0) \\ &= C_1 V_1 + C_2 V_2\end{aligned}$$

When  $\phi_2$  is high  $\rightarrow$

$$\text{Total charge} = C_1(V_1 - V_c) + C_2(V_2 - V_c) + C_3(V_3 - V_c)$$

Charge in  $\phi_1$  = Charge in  $\phi_2$  phase

$$C_1 V_1 + C_2 V_2 = C_1(V_1 - V_c) + C_2(V_2 - V_c) + C_3(V_3 - V_c)$$

$$C_1 \cancel{V_1} + C_2 \cancel{V_2} = C_1 \cancel{V_1} + C_2 \cancel{V_2} + C_3 V_3 - V_c(C_1 + C_2 + C_3)$$

$$V_c = \frac{C_3 V_3}{C_1 + C_2 + C_3}$$


# **Transients in circuits with R,C and switches**

→ Final Condition in RC Circuits →

Points to remember →


- 1) In steady state, Capacitor behaves as an open circuit for DC Input
- 2) To change voltage across capacitor instantaneously, it requires infinite current via it
- 3) In steady state inductor behaves as a short circuit for DC Input
- 4) To change current via inductor instantaneously it requires infinite voltage across it.

Q1.

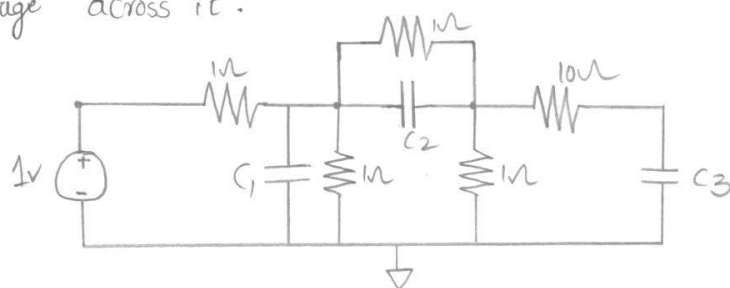

for above circuit calculate voltage that each capacitor gets charged to in a steady state

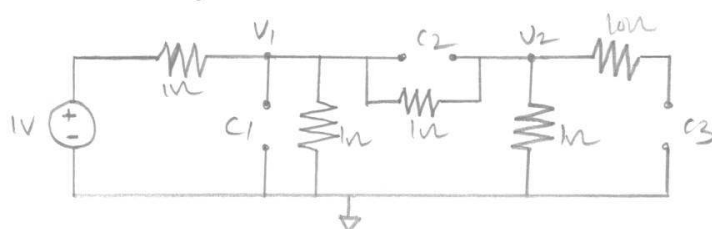Sol<sup>n</sup>. In steady state above circuit will look like



Apply KCL at node 1

$$\frac{(V_1 - 1)}{1} + \frac{V_1}{1} + \frac{V_1 - V_2}{1} = 0$$

KCL at node 2 →

$$\frac{V_2 - V_1}{1} + \frac{V_2}{1} = 0$$

$$V_2 = \frac{1}{2} V_1$$

$$3V_1 = 1 + V_2$$

$$3V_1 - V_2 = 1$$

$$3V_1 - \frac{1}{2}V_1 = 1 \Rightarrow V_1 = \frac{2}{5}V$$

$$\& \quad V_2 = \frac{1}{5}V$$



So,  $C_1$  will get charged

$$V_1 = 2/5$$

$$C_2 \rightarrow V_1 - V_2 = \frac{2}{5} - \frac{1}{5} = \frac{1}{5}V$$

$$C_3 \rightarrow V_2 = \frac{1}{5}V$$

Q2.

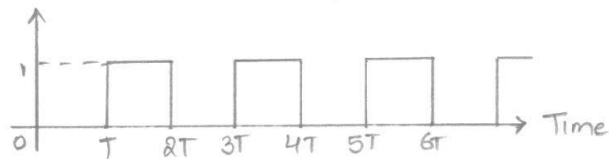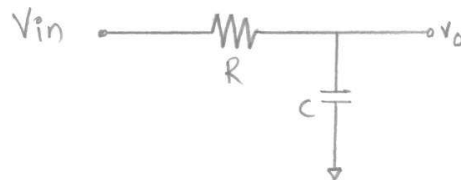

In RC Circuit, Square wave as shown above, is applied.  
plot output waveform for:

$$\text{Case I} \rightarrow RC \ll T$$


$$\text{Case II} \rightarrow RC \gg T$$

under steady state condition

Sol:


Case I)  $\rightarrow RC \ll T$

$\rightarrow$  RC is a time Constant of a circuit. If RC time Constant is less than Square wave time period, output waveform will settle down to input level & will look like.

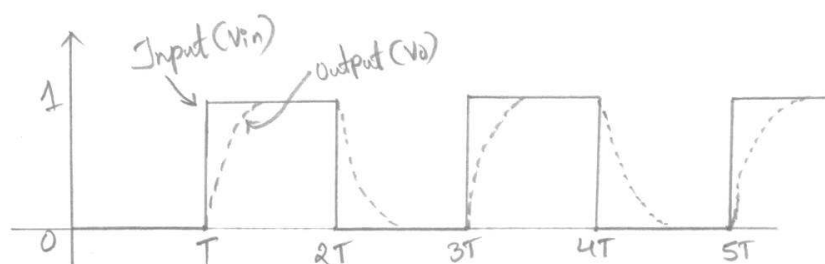


Case II)  $\rightarrow RC \gg T$

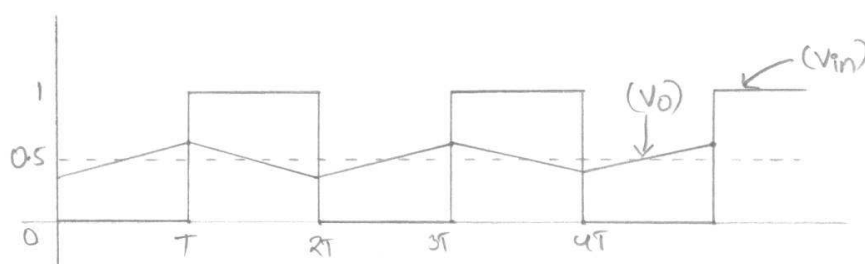$\rightarrow$  If RC time Constant is <sup>larger</sup> ~~less~~ than T, then Circuit will not respond much to the input but under steady state, this circuit will settle to equivalent DC level of an input



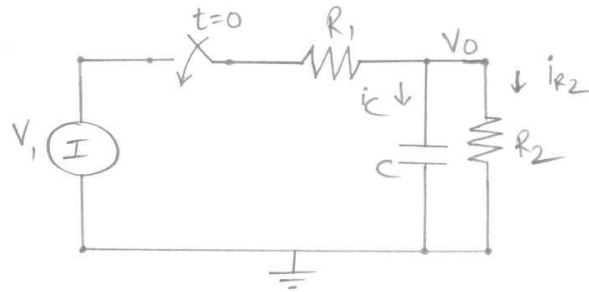Q.1 Plot  $V_o, i_c, i_{R_2}$  for the circuit shown below, if the Switch <sup>①</sup> is closed at  $t=0$



For  $t > 0$ , writing KCL for the output node,

$$\frac{V_o}{R_2} + C \cdot \frac{dV_o}{dt} + \frac{V_o}{R_1} = \frac{V_1}{R_1}$$

$$\frac{dV_o}{dt} + \frac{V_o}{C} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_1}{R_1 C} \quad \text{--- (1)}$$

The solution to the above equation is found by solving the characteristic equation ( $V_1 = V_1 = 0$ )

$$\frac{dV_o}{dt} + \frac{V_o}{C} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = 0 \quad \text{--- (2)}$$

The solution to eq<sup>n</sup> (2) can be of the form

$$V_o = K e^{-t/\tau} + C_1 \quad \text{where } K \text{ \& } C_1 \text{ are constants}$$

$$\text{At } t=0^+ \quad V_o = 0 \quad \tau = C \left( \frac{R_1 R_2}{R_1 + R_2} \right) = C(R_1 || R_2)$$

$$0 = K + C_1$$

$$K = -C_1$$

$$\text{At } t=\infty \quad V_o = \frac{V_1 R_2}{R_1 + R_2}$$

$$\frac{V_1 \cdot R_2}{R_1 + R_2} = C_1 \Rightarrow k = \frac{-V_1 R_2}{R_1 + R_2}$$

Therefore,

$$V_0 = \frac{V_1 R_2}{R_1 + R_2} (1 - e^{-t/\tau})$$




$$i_c = \frac{C \cdot dV_0}{dt} = C \cdot \frac{V_1 \cdot R_2}{R_1 + R_2} \cdot \frac{1}{\tau} \cdot e^{-t/\tau}$$

$$i_c = \frac{V_1}{R_1} e^{-t/\tau}$$

$$i_{R_2} = \frac{V_0}{R_2} = \frac{1}{R_2} \cdot \frac{V_1 \cdot R_2}{R_1 + R_2} \cdot (1 - e^{-t/\tau})$$


$$= \frac{V_1}{R_1 + R_2} (1 - e^{-t/\tau})$$

$\approx$   ~~$\frac{V_1}{R_1}$~~

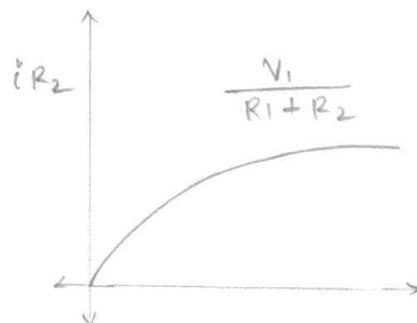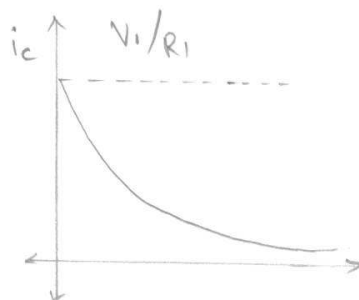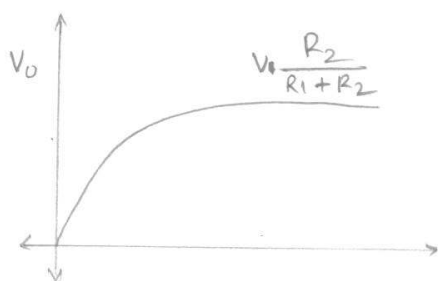



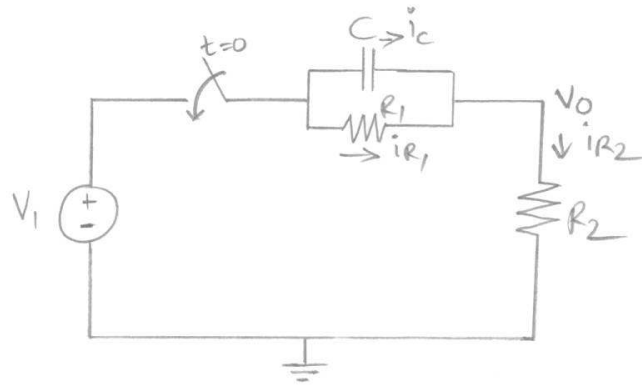Q2 If the Switch is closed at  $t=0$ , plot  $V_o, i_c, i_{R_1}, i_{R_2}$  ③



For  $t > 0$ , Writing KCL for output node,

$$\frac{V_o}{R_2} + \frac{V_o}{R_1} + C \frac{dv_o}{dt} = \frac{V_1}{R_1} + C \frac{dv_1}{dt}$$

$$\frac{dv_o}{dt} + \frac{V_o}{C} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_1}{R_1 C} + \frac{dv_1}{dt}$$

$\frac{dv_1}{dt} = 0, v_1 = 0$  gives us the Characteristic equation

$$\frac{dv_o}{dt} + \frac{V_o}{C} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = 0$$

$$\therefore V_o = k e^{-t/\tau} + C_1 \text{ where } k, C_1 \text{ are Constants}$$

$$\tau = C \cdot \frac{R_1 R_2}{R_1 + R_2} = C(R_1 || R_2)$$

At  $t=0$ ,  $C$  appears like a Short ckt

$$V_o = V_1$$

$$V_1 = k + C_1$$

At  $t=\infty$ ,  $C$  appears like open ckt

$$V_o = V_1 \cdot \frac{R_2}{R_1 + R_2} = 0 + C_1$$

$$C_1 = V_1 \cdot \frac{R_2}{R_1 + R_2}$$

$$K = V_1 \frac{R_1}{R_1 + R_2}$$

$$\therefore V_0 = \frac{V_1 R_1}{R_1 + R_2} \cdot e^{-t/\tau} + V_1 \cdot \frac{R_2}{R_1 + R_2}$$





$$V_0 = \frac{V_1}{R_1 + R_2} (R_1 e^{-t/\tau} + R_2)$$

$$i_c = C \cdot \frac{d}{dt} (V_1 - V_0) = C \cdot \frac{V_1}{R_1 + R_2} \cdot R_1 \frac{1}{\tau} \cdot e^{-t/\tau}$$


$$i_c = \frac{V_1}{R_2} \cdot e^{-t/\tau}$$

$$i_{R_1} = \frac{V_1 - V_0}{R_1} = \frac{V_1}{R_1 + R_2} (1 - e^{-t/\tau})$$
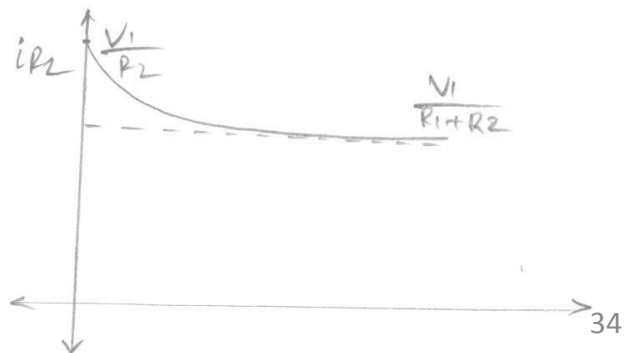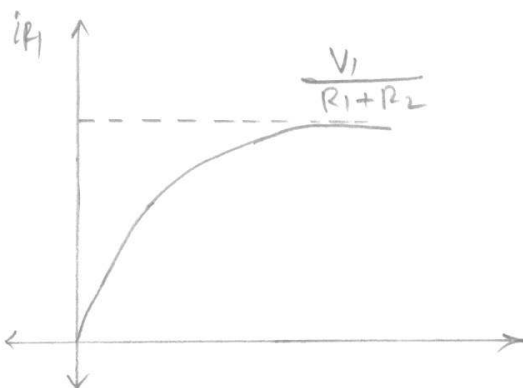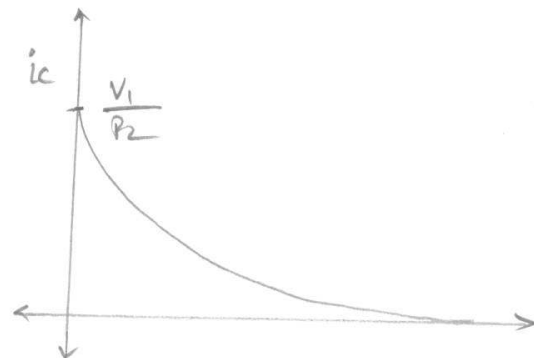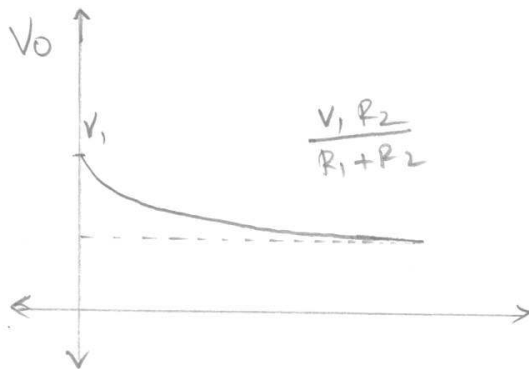
$$i_{R_2} = \frac{V_0}{R_2} = \frac{V_1}{R_1 + R_2} \left( \frac{R_1}{R_2} \cdot e^{-t/\tau} + 1 \right)$$



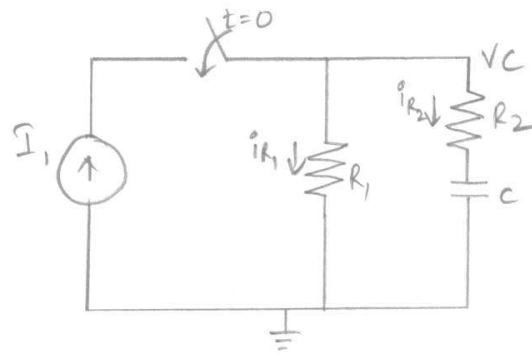Q<sub>3</sub>. For the ckt shown below, if the switch is closed ⑤ at  $t=0$ , plot  $V_C$ ,  $i_{R_2}$ ,  $i_{R_1}$






Sol<sup>n</sup>


$$V_C = I_1 R_1 (1 - e^{-t/\tau}) \quad \text{where } \tau = (R_1 + R_2) \cdot C$$

$$i_{R_2} = I_1 \cdot \frac{R_1}{R_1 + R_2} \cdot e^{-t/\tau}$$
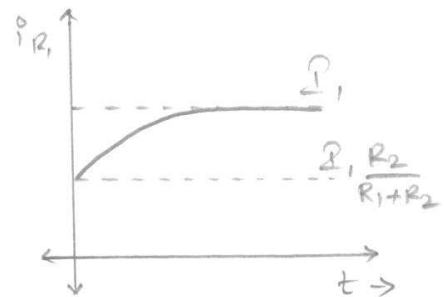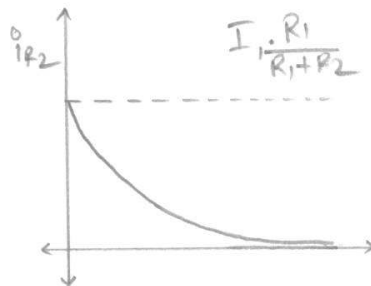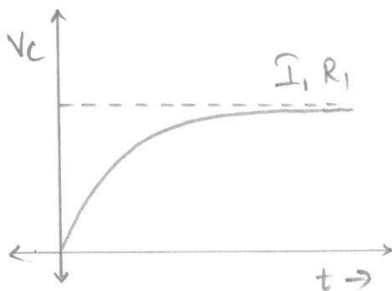
$$i_{R_1} = I_1 \left( 1 - \frac{R_1}{R_1 + R_2} \cdot e^{-t/\tau} \right)$$





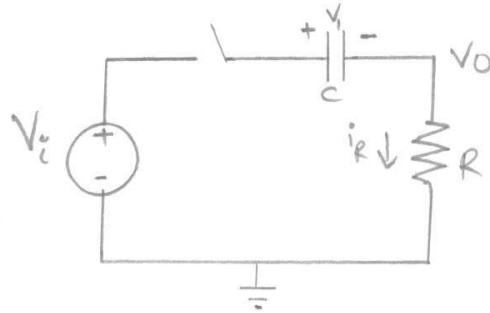Qy. For the Circuit shown below, if the voltage across the capacitor is  $V_1$  at  $t=0^-$  and the Switch is closed at  $t=0$ , plot  $V_0$ ,  $i_R$  for  $t > 0$




$$V_0 = (V_i - V_1) e^{-t/\tau} \quad \text{where } \tau = RC$$
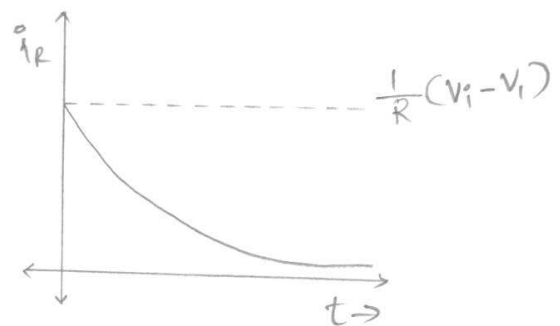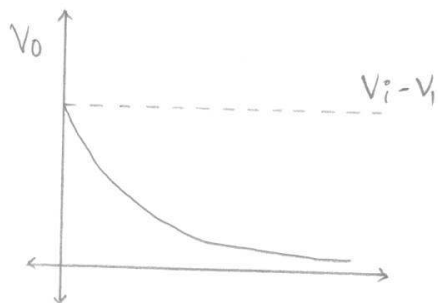
$$i_R = \frac{1}{R} (V_i - V_1) e^{-t/\tau}$$



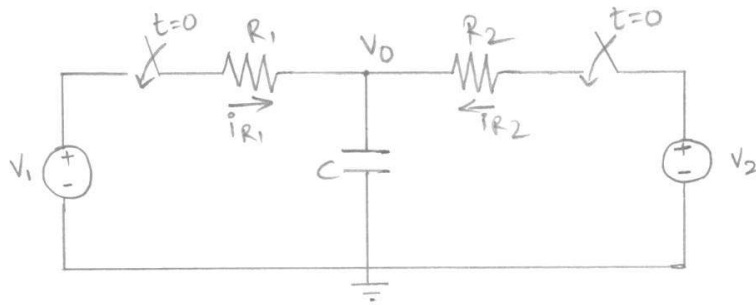Q5. For the circuit shown below, if both the switches are closed at  $t=0$ , plot  $V_0$ ,  $i_{R_1}$ ,  $i_{R_2}$



Sol<sup>n</sup>

$$V_0 = V_{ss}(1 - e^{-t/\tau}) \quad \text{where } \tau = C(R_1 \parallel R_2)$$


$$V_{ss} = V_1 \cdot \frac{R_2}{R_1 + R_2} + V_2 \cdot \frac{R_1}{R_1 + R_2}$$

$$i_{R_1} = \frac{V_1 - V_2}{R_1 + R_2} + \frac{V_{ss}}{R_1} \cdot e^{-t/\tau}$$


$$i_{R_2} = \frac{V_2 - V_1}{R_1 + R_2} + \frac{V_{ss}}{R_2} \cdot e^{-t/\tau}$$

8

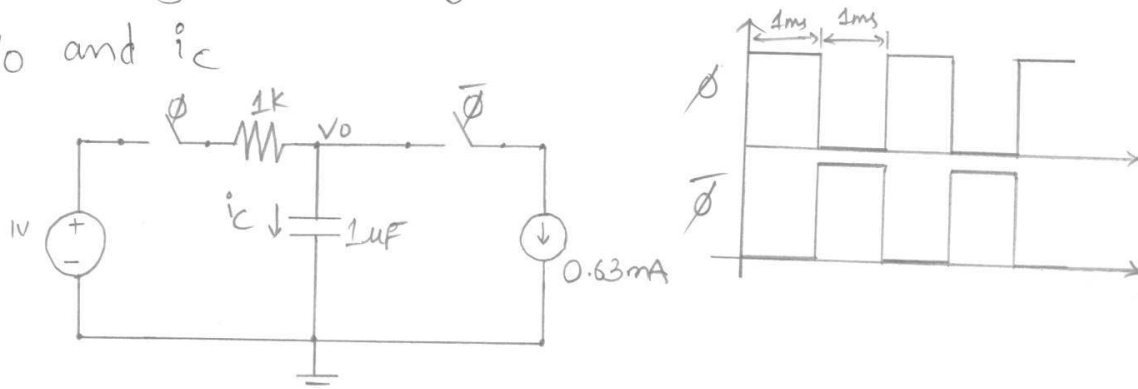Q6. For the Circuit shown below, if the Switches are Operated using Complementary clocks  $\phi$  and  $\bar{\phi}$  as shown plot  $V_o$  and  $i_c$




Sol<sup>n</sup>.

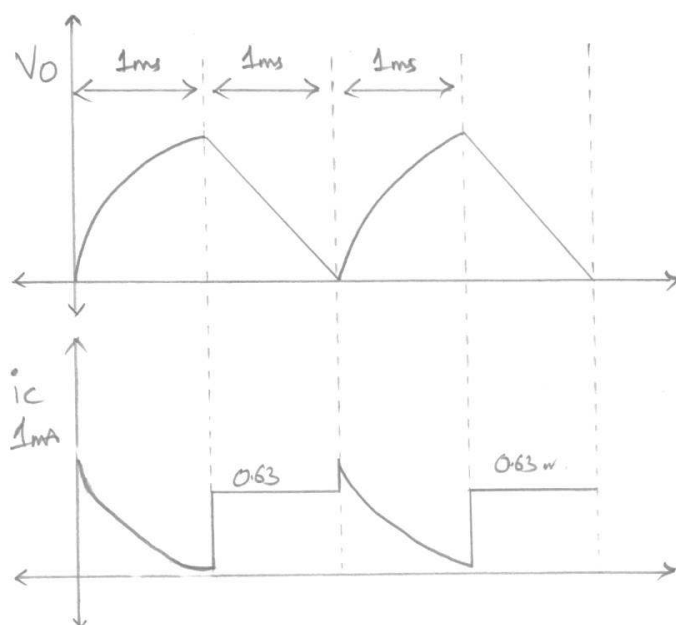

Q7. Plot  $V_o, i_c$  for the Circuits shown below

9

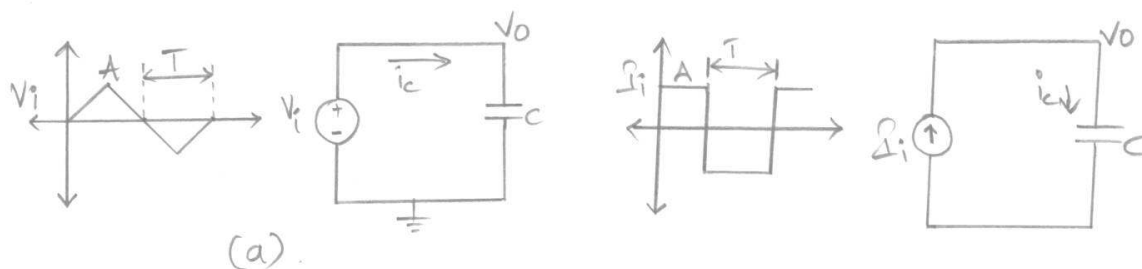


a) For a Capacitor,  $i_c = C \cdot \frac{dv_c}{dt}$   
 $V_c = V_i \Rightarrow i_c = C \cdot \frac{dv_i}{dt} \dots \dots (1)$

Equation (1) indicates a useful property of a capacitor, the Capacitor Current is a derivative of the Voltage across it. This Property is utilised in many circuits for waveform generation

For (a),  $V_i = \frac{2A}{T}t$  for  $0 < t < \frac{T}{2}$   
 $= 2A - \frac{2A}{T}t$  for  $\frac{T}{2} < t < \frac{3T}{2}$

Using eqn (1)

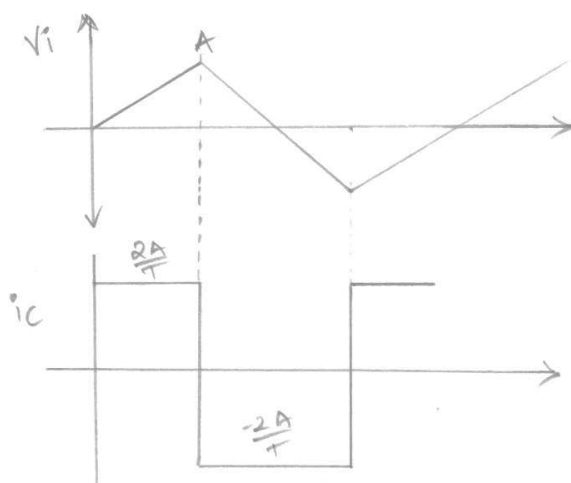$i_c = \frac{2A}{T}$  for  $0 < t < \frac{T}{2}$   
 $= -\frac{2A}{T}$  for  $\frac{T}{2} < t < \frac{3T}{2}$



$V_c = V_i$

for a capacitor,  $V_c = \frac{1}{C} \int_0^t I_i \cdot dt + V_c^{0-} \quad \text{--- (2)}$

Where  $V_c^{0-}$  is the initial voltage on Capacitor

Equation(2) Shows that the Current flowing into a Capacitor is integrated to develop the voltage across it. This is a very useful property utilised in many Circuits

$$I_i = I_1 \quad \text{for } 0 < t < \frac{T}{2}$$

$$= -I_1 \quad \text{for } \frac{T}{2} < t < \frac{3T}{2}$$


Using eq<sup>n</sup>(2) and assuming that initial voltage  $V_c^{0-}$  on the Capacitor

is zero.

$$V_c = \frac{1}{C} \int_0^t I_i \cdot dt = \frac{I_1}{C} \cdot t \quad \text{for } 0 < t < \frac{T}{2}$$

$$= \frac{1}{C} \int_{T/2}^t (-I_1) \cdot dt = -\frac{I_1}{C} \cdot t + \frac{I_1}{C} \cdot \frac{T}{2} \quad \frac{T}{2} < t < \frac{3T}{2}$$



$$i_c = I_i$$

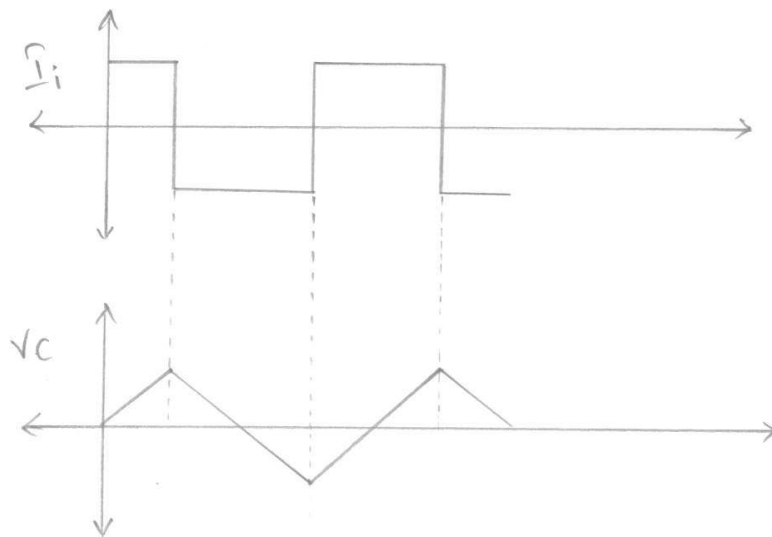





11

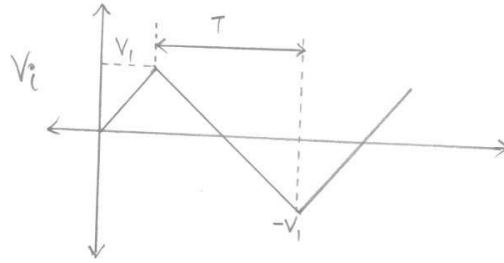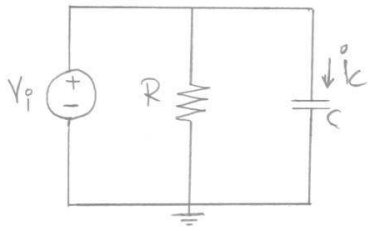Q.8. Plot  $i_c$  for the circuit shown below



Sol<sup>n</sup>  $\rightarrow$  Same as Q.7(a)

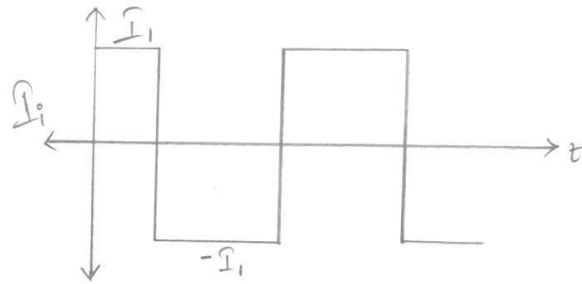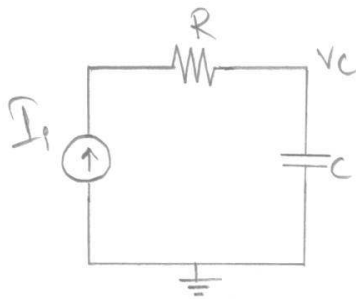Q.9 Plot  $v_c$  for the circuit shown below



Sol<sup>n</sup>  $\rightarrow$  Same as Q.7(b)

Q.10 Plot  $v_o$  for the circuit shown below

